
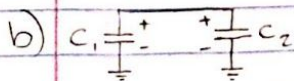


# 1. MP3 Player

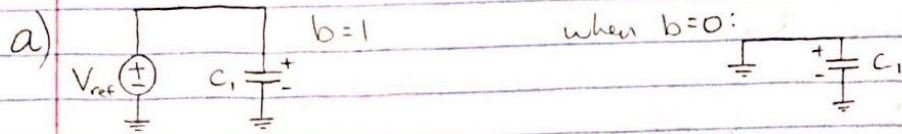

c) step 3: phase 1:  
 $V_{n1}$  connected to ground, so  $V_{n1} = 0V$

phase 2:

$$V_2 = \frac{V_{ref}}{2} \text{ and } V_1 = 0$$

$$Q_{C2i} = Q_{C2f} + Q_{C1f}$$

$$C_2 \frac{V_{ref}}{2} = C_2 V_{n2} + C_1 V_{n2}$$

$$C \frac{V_{ref}}{2} = 2C V_{n2}$$

$$V_{n2} = \frac{V_{ref}}{4}$$

step 4: phase 1:

$V_{n1}$  connected to  $V_{ref}$ , so  $V_{n1} = V_{ref}$

phase 2:

$$V_1 = V_{ref} \text{ and } V_2 = \frac{V_{ref}}{4}$$

$$Q_{C1i} + Q_{C2i} = Q_{C1f} + Q_{C2f}$$

$$C_1 V_{ref} + C_2 \frac{V_{ref}}{4} = C_1 V_{n2} + C_2 V_{n2}$$

$$\frac{5}{4} V_{ref} C = 2C V_{n2}$$

$$V_{n2} = \frac{5}{8} V_{ref}$$

Step	b	$V_{n1}$	$V_{n2}$
1	0	0V	0V
2	1	$V_{ref}$	$\frac{V_{ref}}{2}$
3	0	0V	$\frac{V_{ref}}{4}$
4	1	$V_{ref}$	$\frac{5}{8} V_{ref}$



d) step 4: phase 2:

$$V_{n2} = \frac{13V_{ref}}{16}$$

assuming step 4 has  $b=1$

$$C_1 V_{ref} + C_2 V = (C_1 + C_2) V_{n2}$$

$$V = \frac{1}{C_2} (C_1 + C_2) V_{n2} - C_1 V_{ref} = \frac{C_1}{C_2} V_{n2} + V_{n2} - \frac{C_1}{C_2} V_{ref}$$

$$V = \frac{C_1}{C_2} \frac{13}{16} V_{ref} + \frac{13}{16} V_{ref} - \frac{C_1}{C_2} V_{ref} = \frac{13}{16} V_{ref} - \frac{3}{16} V_{ref}$$

$$V = \frac{5}{8} V_{ref}$$

step 3: phase 2:

$$V_{n2} = \frac{5}{8} V_{ref}$$

$V_{n2} = \frac{5}{8} V_{ref}$  is equal to  $V_{n2}$  of step 4 in part (c)

So, this sequence's steps 1-3 are same as steps 2-4 from part (c).


So, the bit sequence is 1011

Step	b
1	1
2	0
3	1
4	1





## 2. Integration using Op-Amps

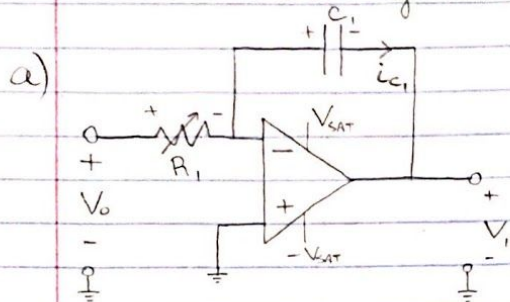

$$I_{R_i} = i_{C_i} = C_i \frac{dV_{C_i}}{dt}$$

$$I_{R_i} = C_i \frac{-dV_i}{dt}$$

$$-\frac{dV_i}{dt} = \frac{I_{R_i}}{C_i}$$

$$V_i = -\frac{I_{R_i}}{C_i} t$$

$$V_i = -\frac{V_o}{C_i R_i} t$$


$$\text{slope} = -\frac{V_o}{C_i R_i}$$

b)  $i_{C_i} = C_i \frac{dV_{C_i}}{dt}$

Doubling  $C_i$  doubles the current through  $C_i$ .

But, the slope is twice smaller when  $C_i$  is doubled

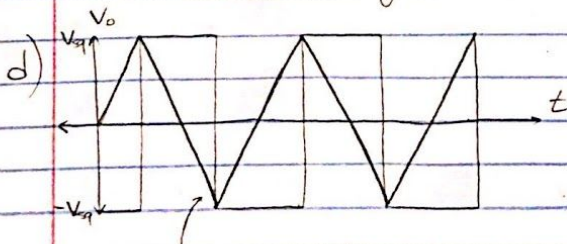c) If we connect a load resistor, then  $V_i$  doesn't change. This is because we have an op-amp connected in negative feedback.




$$\text{slope} = -\frac{V_{sat}}{C_i R_i}$$



### 3. Cool for the Summer

a)

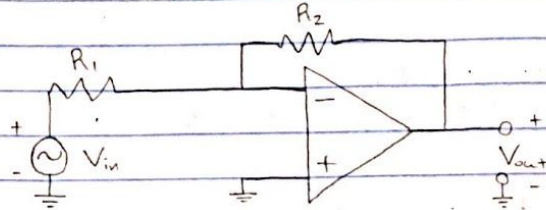

$$I_{R_1} = I_{R_2}$$

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2}$$

$$-V_{out} = V_{in} \frac{R_2}{R_1}$$

$$V_{out} = -V_{in} \frac{R_2}{R_1}$$

b)

$$I_{R_{s1}} + I_{R_{s2}} = I_{R_2}$$


$$\frac{V_{s1}}{R_{s1}} + \frac{V_{s2}}{R_{s2}} = -\frac{V_{out}}{R_2}$$

$$V_{out} = -R_2 \left( \frac{V_{s1}}{R_{s1}} + \frac{V_{s2}}{R_{s2}} \right)$$

$$c) -\left( \frac{R_2}{R_{s1}} V_{s1} + \frac{R_2}{R_{s2}} V_{s2} \right) = -\left( \frac{1}{4} V_{s1} + 2 V_{s2} \right)$$

If  $R_2 = 2\Omega$ ,  $R_{s1} = 8\Omega$ , and  $R_{s2} = 1\Omega$ , then the desired relationship works. There are more than 1 way.

d)

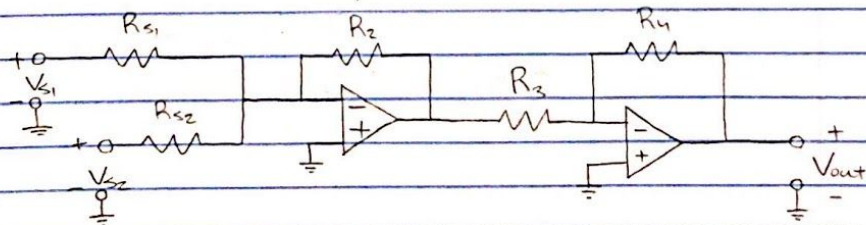


$$V_{out} = -\frac{12}{12} V_{in}$$

$$R_3 = R_4$$



#### 4. PetBot Design

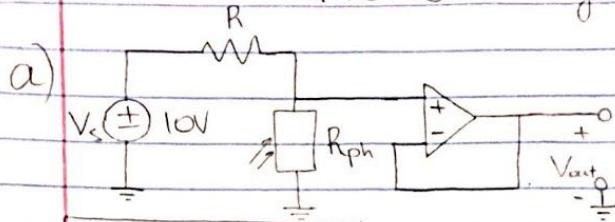

$$V_{out} = V_s \frac{R_{ph}}{R_{ph} + R}$$

when close to light:  $5V \leq 10V \frac{10k\Omega}{10k\Omega + R}$

$$\frac{1}{2}(10k\Omega + R) \leq 10k\Omega$$

$$R \leq 10k\Omega$$


So,  $V_{out} = 10V \frac{R_{ph}}{R_{ph} + 10k\Omega}$

b)

$$V_{out} = V_1 + V_2$$

at  $R_{ph} = 1k\Omega$ :  $V_1 = -V_2$

$$V_s = 10V$$

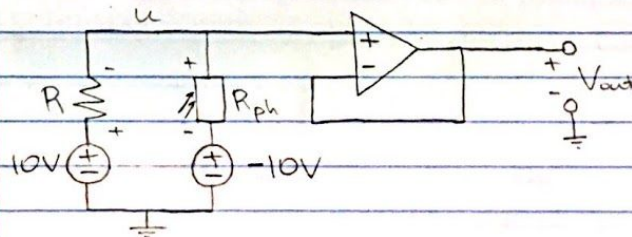

at  $u$ : superposition

$$u = \frac{10V R_{ph}}{R_{ph} + R} - \frac{10V R}{R + R_{ph}} = \frac{10V}{R_{ph} + R} (R_{ph} - R)$$


at  $R_{ph} = 1k\Omega$ :  $u = 0$ , so  $R = 1k\Omega$

$$V_{out} = \frac{10V R_{ph}}{R_{ph} + 1k\Omega} - \frac{(10V)(1k\Omega)}{1k\Omega + R_{ph}}$$

$$V_{out} = \frac{V_s R_{ph}}{R_{ph} + R} - \frac{V_s R}{R_{ph} + R} = V_s \frac{R_{ph} - R}{R_{ph} + R}$$

## 5. Op Amp Nodal Analysis

a)

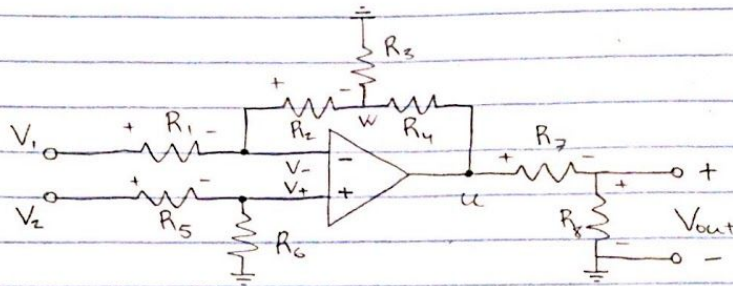

b)

$$I_{R7} = I_{R8}$$

$$\frac{u - V_{out}}{R7} = \frac{V_{out}}{R8}$$

$$u R8 - V_{out} R8 = R7 V_{out}$$

$$V_{out} = \frac{u R8}{R8 + R7}$$

$$V_+ = V_2 \frac{R6}{R5 + R6} = V_-$$

$$I_{R2} = I_{R3} + I_{R4}$$

$$\frac{V_- - w}{R2} = \frac{w}{R3} + \frac{w - u}{R4}$$

$$R3 R4 (V_- - w) = R2 R4 w + R2 R3 (w - u)$$

$$w (R2 R4 + R2 R3 + R3 R4) = R3 R4 V_- + R2 R3 u$$

$$u = \frac{1}{R2 R3} [w (R2 R4 + R2 R3 + R3 R4) - R3 R4 V_-]$$

$$I_{R1} = I_{R2}$$

$$\frac{V_1 - V_-}{R1} = \frac{V_- - w}{R2}$$

$$V_1 R2 - V_- R2 = V_- R1 - w R1$$

$$w R1 = V_- (R1 + R2) - V_1 R2$$

$$w = \frac{R1 + R2}{R1} \cdot \frac{V_2 R6}{R5 + R6} - V_1 R2$$

$$u = w \left( \frac{R4}{R3} + 1 + \frac{R4}{R2} \right) - \frac{R4}{R2} \cdot V_2 \frac{R6}{R5 + R6}$$

$$u = \left( \frac{V_2 R6 (R1 + R2)}{R1 (R5 + R6)} - V_1 R2 \right) \left( \frac{R4}{R3} + \frac{R4}{R2} + 1 \right) - \frac{V_2 R4 R6}{R2 (R5 + R6)}$$

$$V_{out} = u \frac{R8}{R8 + R7}$$


$$V_{out} = \frac{R8}{R8 + R7} \left[ \left( \frac{V_2 R6}{R5 + R6} + \frac{V_2 R6 R2}{R1 (R5 + R6)} - V_1 R2 \right) \left( \frac{R4}{R3} + \frac{R4}{R2} + 1 \right) - \frac{V_2 R4 R6}{R2 (R5 + R6)} \right]$$





$$c) R_{th} = \frac{V_{out}}{I_{sc}} = \frac{U \cdot \frac{R_2}{R_1 + R_2}}{\frac{U}{R_2}}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

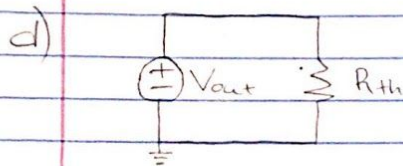

## 6. Homework Process

I worked on this homework alone. I read all the notes and was able to do the problems.

